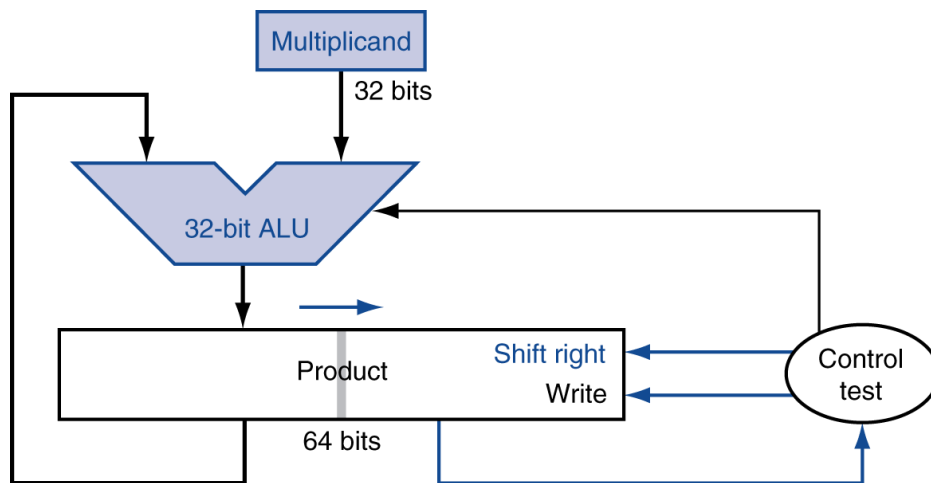


Optimized Multiplier Example




Show the register content for multiplying 6 by 4

Multiplicand remains fixed at 4 = 0100

	Product	Notes
init	0000 0110	LSB=0 → shift right
1	0100 0011	LSB=1 → addition then shift right
2	0110 0001	LSB=1 → addition then shift right
3	0011 0000	LSB=0 → shift right
4	0001 1000	Result = 24

Optimized Divider Example

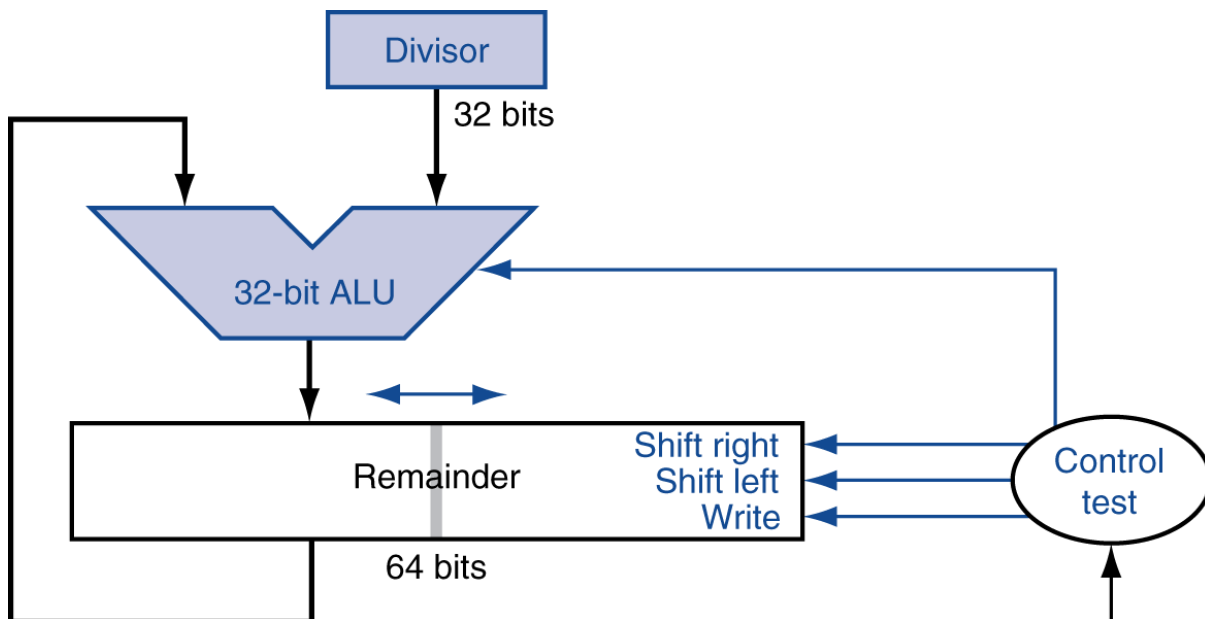

Show the register content for dividing 13 by 3

Divisor = 3 = 0011

	Remainder before	Remainder after	Notes
init		0000 1101	
1	0001 101X	0001 1010	Shift left → Subtraction res is -ve → restore and quotient bit = 0
	1110 101X		
2	0011 010X	0000 0101	Shift left → Subtraction res is +ve → quotient bit = 1
	0000 010X		
3	0000 101X	0000 1010	Shift left → Subtraction res is -ve → restore and quotient bit = 0
	1101 101X		
4	0001 010X	0001 0100	Shift left → Subtraction res is -ve → restore and quotient bit = 0
	1110 010X		
	Remainder= 0001=1 quotient=0100 = 4		