

# Discussion

- Explain what is the meant by the design principal “make the common case fast.” Considering MIPS processor, identify a design choice that uses this principal. Identify a special case (an uncommon case) and explain how MIPS handle it.
- Floating point number representation involves splitting the data unit (e.g., word) into multiple fields. What are these fields? How the stored value is calculated? How would changing the size of these fields affect the number precision and range?
- The principal of “performance by prediction” is used in computer design. Identify one case for which this principal is used to improve the performance. Explain how this principal is used to improve the performance.
- It is well-known that the design of computer has a cost-performance tradeoff. Identify two scenarios that confirm this tradeoff and explain the tradeoff aspects.

# The Processor

Dr. Ahmed Zahran

WGB 182

[a.zahran@cs.ucc.ie](mailto:a.zahran@cs.ucc.ie)

# How a processor is designed?

- Processors are designed to execute binary (machine) instructions
- Simple subset, shows most aspects
  - Memory reference: lw, sw
  - Arithmetic/logical: add, sub, and, or, slt
  - Control transfer: beq, j
- We will examine two MIPS implementations
  - A simplified version
  - A pipelined version

# Instruction Execution

- Two basic steps for all instructions


## 1. Instruction fetch

- $PC \rightarrow$  instruction memory,
- $PC \leftarrow$  target address or  $PC + 4$


## 2. Execution

- Read and/or write registers
  - Register numbers  $\rightarrow$  register file,
- Use ALU to calculate
  - Arithmetic result
  - Memory address for load/store
  - Branch target address

# CPU Overview

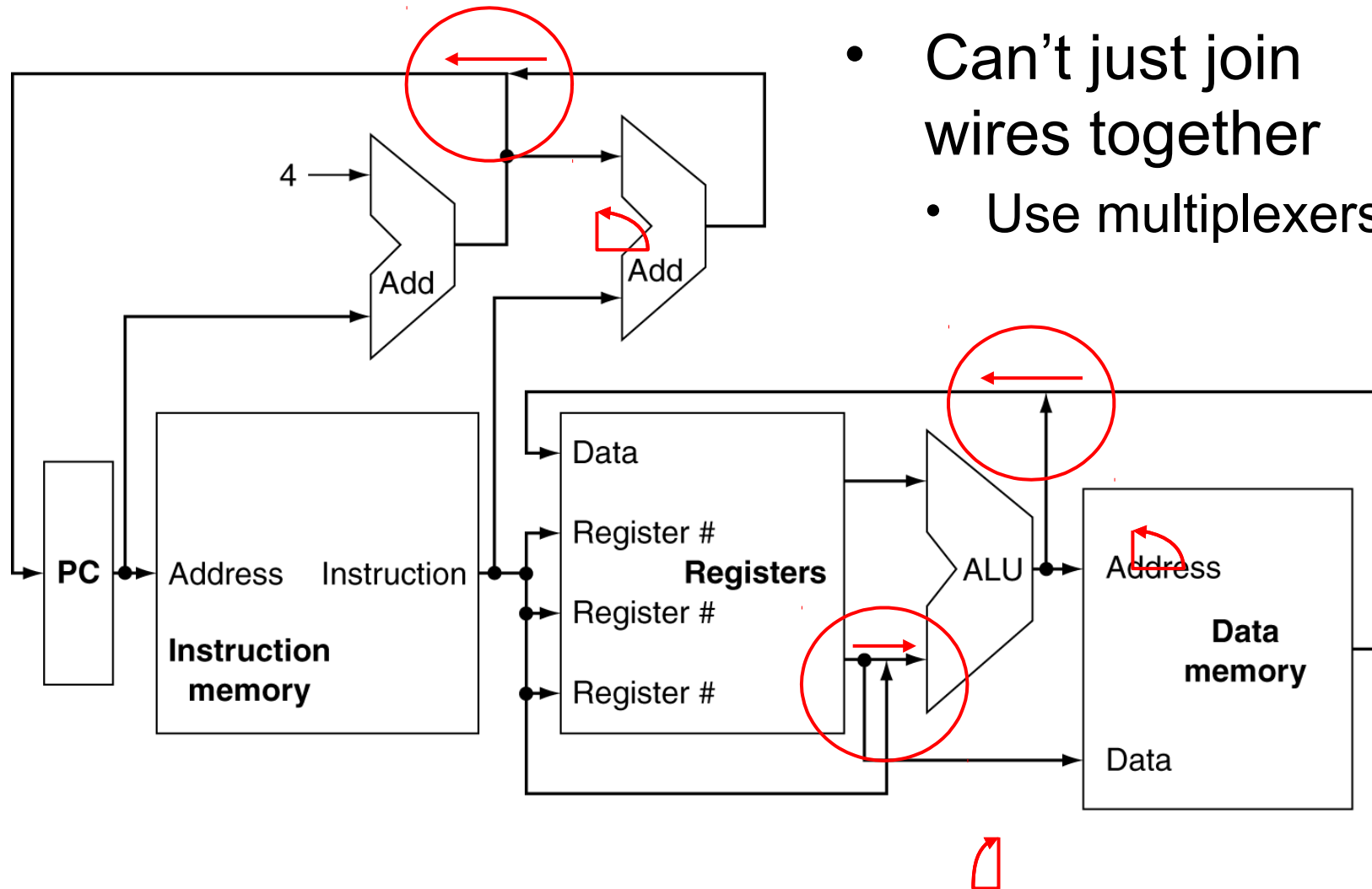


# Control

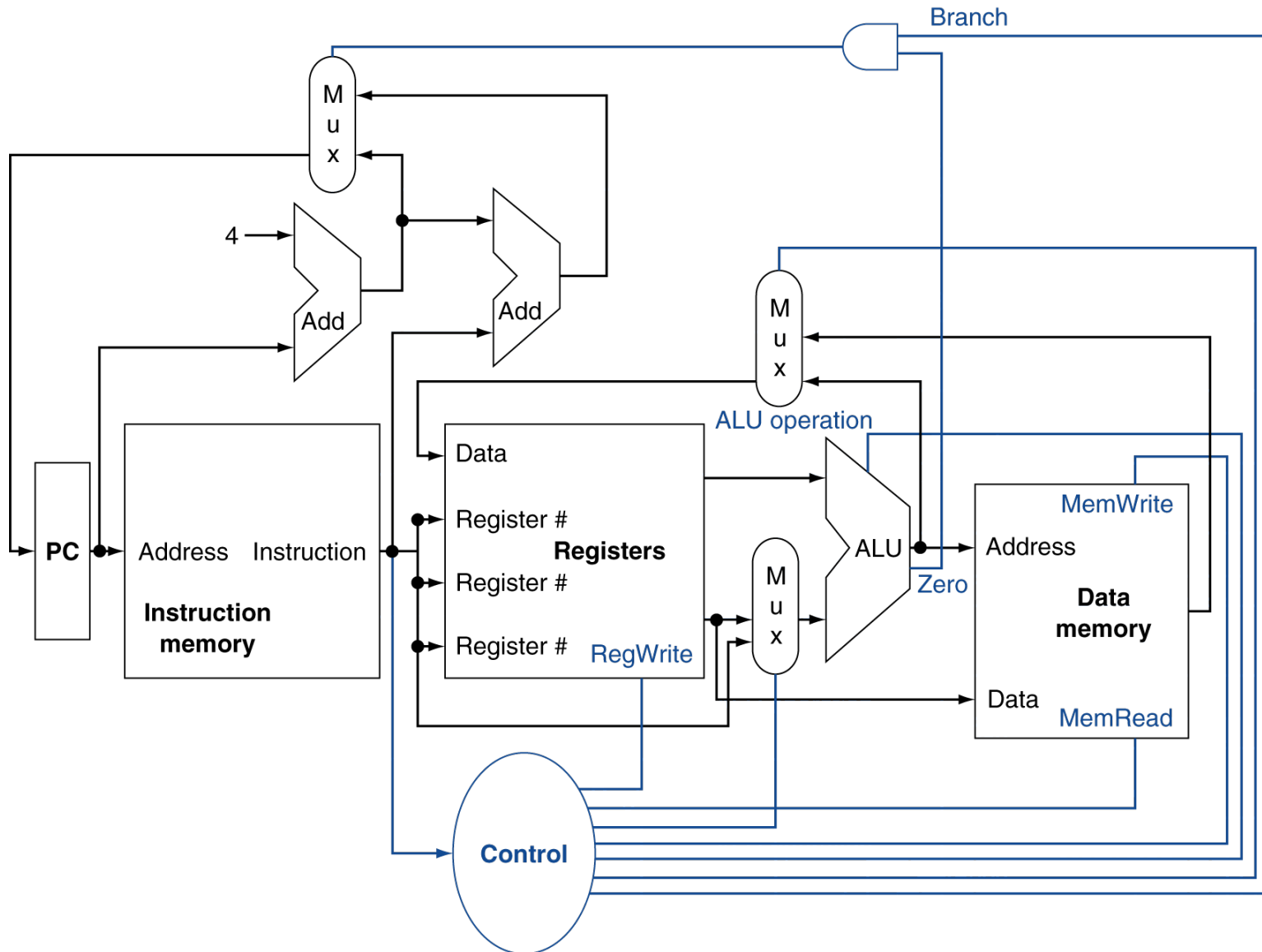

# Processor Components


- Multiplexer

- $Y = S ? I1 : I0$

 


- Arithmetic/Logic Unit

- $Y = F(A, B)$


 


- Logic-gate

- $Y = A \& B$


 


- Sequential elements

  
  
# Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  - Longest delay determines clock period






# MIPS Datapath

# Building a Datapath


- Datapath
  - Components that process data and addresses in the CPU
    - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
  - Identify and connect logic components required by different processor functions
    - Instruction fetch
    - Executing instructions

# Instruction Fetch

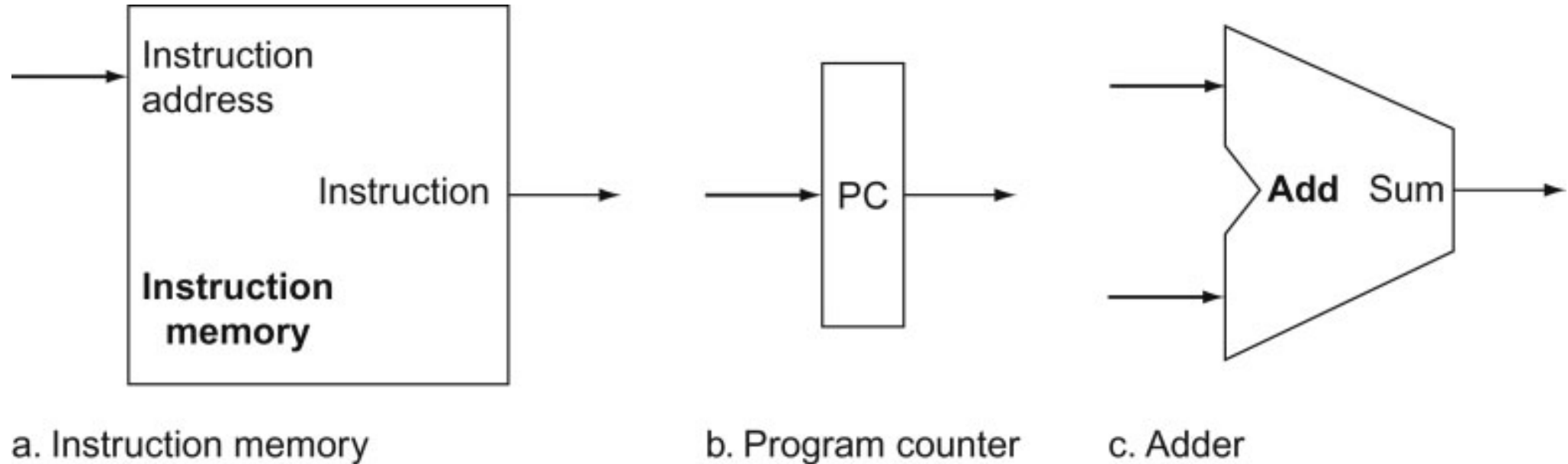


Requires two state elements  
Instruction memory and PC


# Instruction Fetch

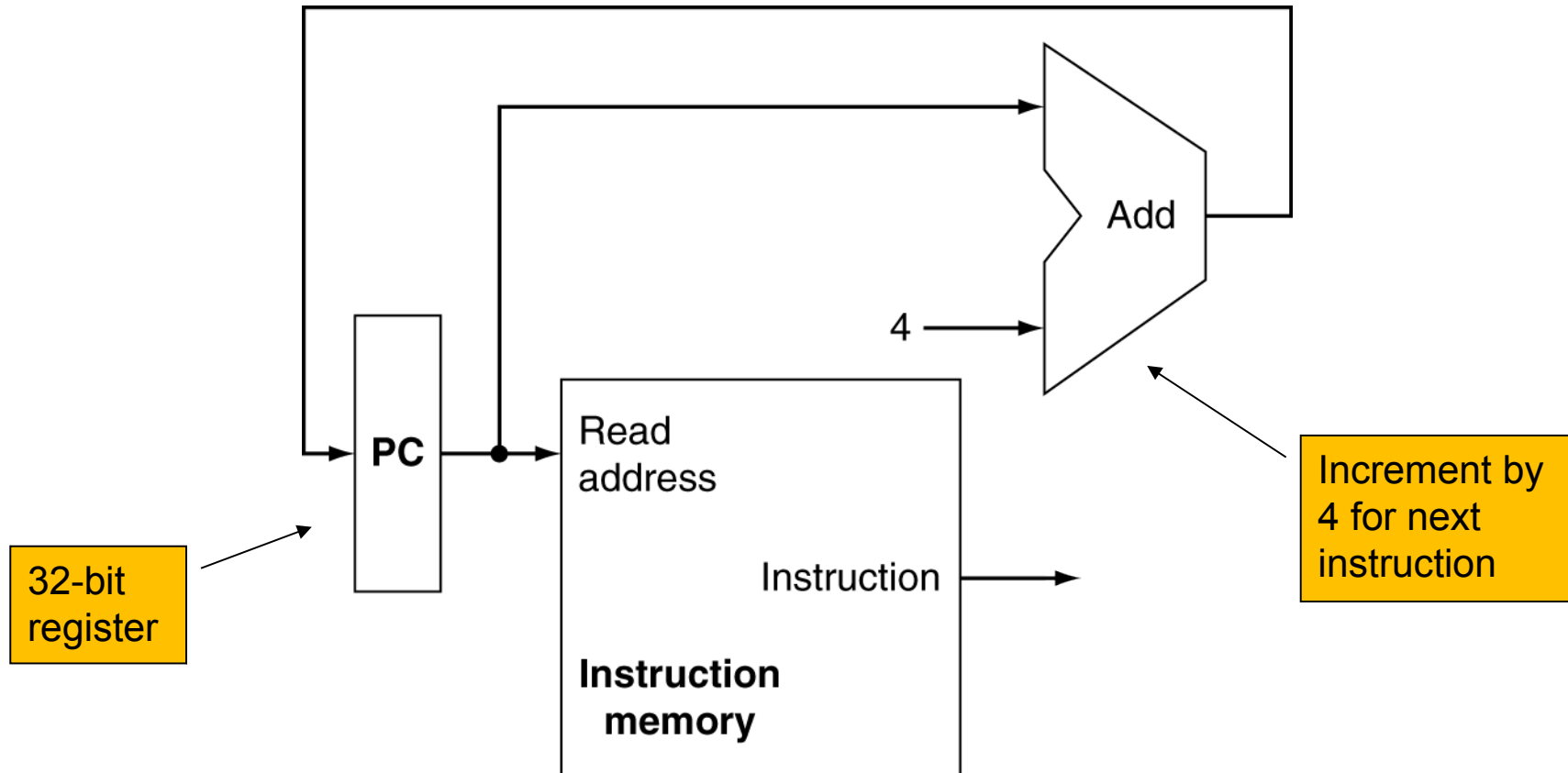


# R-Format Instructions

 

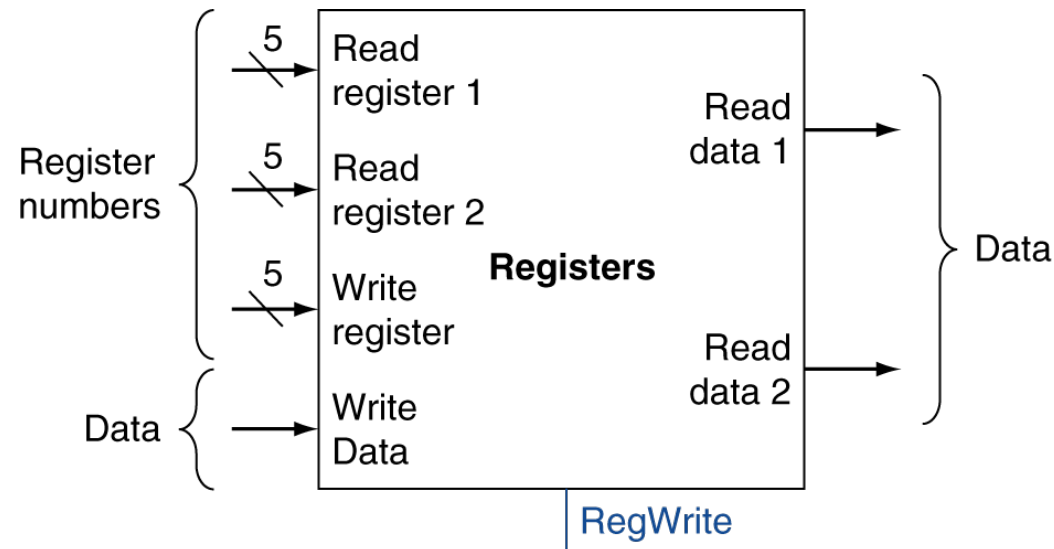- Read two register operands
- Perform arithmetic/logical operation




a. Registers

 


b. ALU


# Load/Store Instructions

 

 - Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register




a. Data memory unit

 


b. Sign extension unit

# Branch Instructions

 

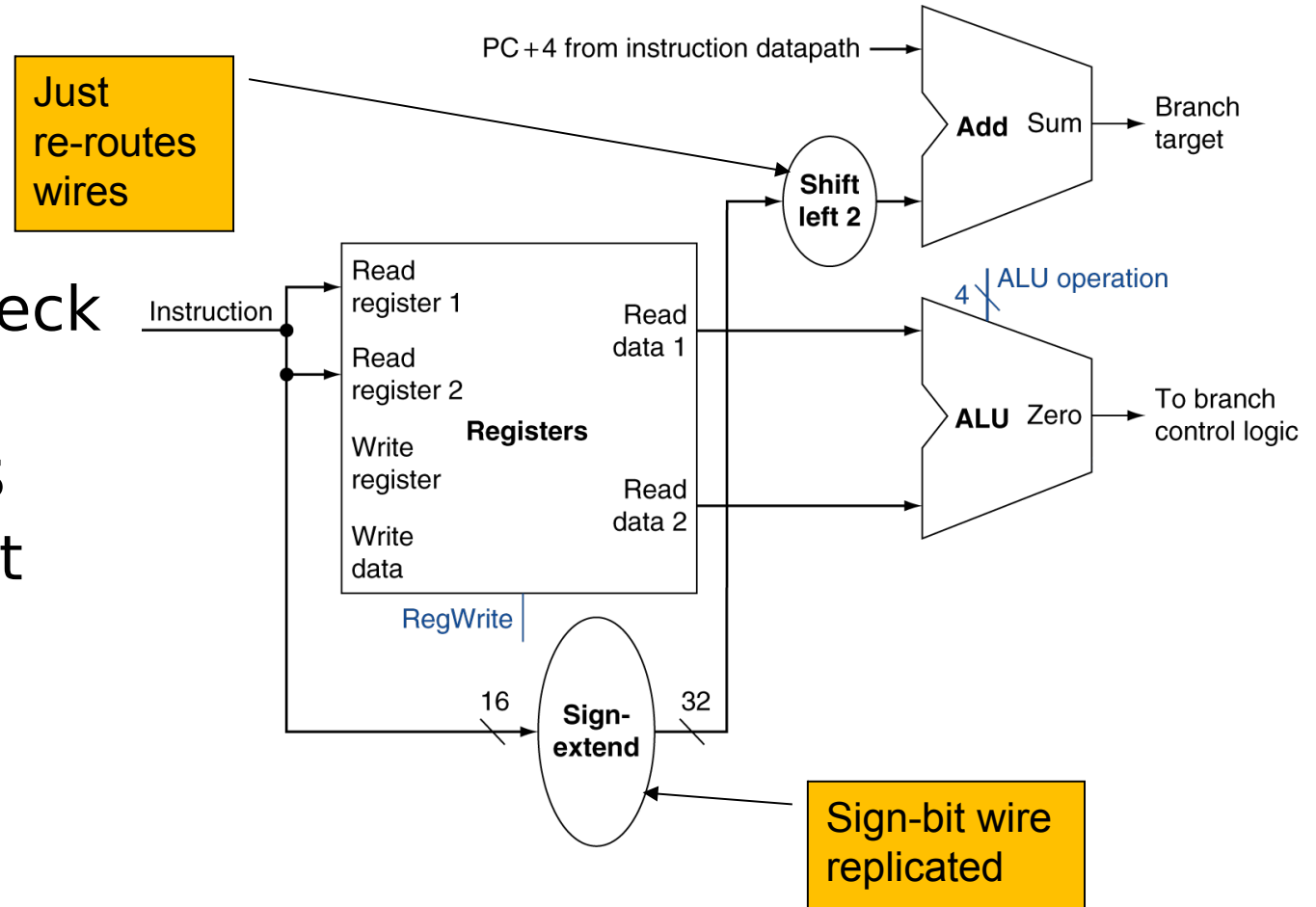- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 2 places (word displacement)
  - Add to PC + 4



# Summary